

Direction-Selective Parallel Module Structure for Cascaded Bridge and Modular Multilevel Converters with Minimum Transistor Count

Jinshui Zhang¹, Stefan Goetz²

^{1,2} Duke University


TABLE OF CONTENT

- Introduction
 - General structure of modular multilevel converter (MMC)
 - Evolution to enable parallel connectivity
- Working principle of Direction-Selective Parallel Structure
 - Structure
 - Conduction mechanism
 - Paralleling mechanism
- Results
- Conclusion

TABLE OF CONTENT

- Introduction
 - General structure of modular multilevel converter (MMC)
 - Evolution to enable parallel connectivity
- Working principle of Direction-Selective Parallel Structure
 - Structure
 - Conduction mechanism
 - Paralleling mechanism
- Results
- Conclusion

MMC IS EVERYWHERE...

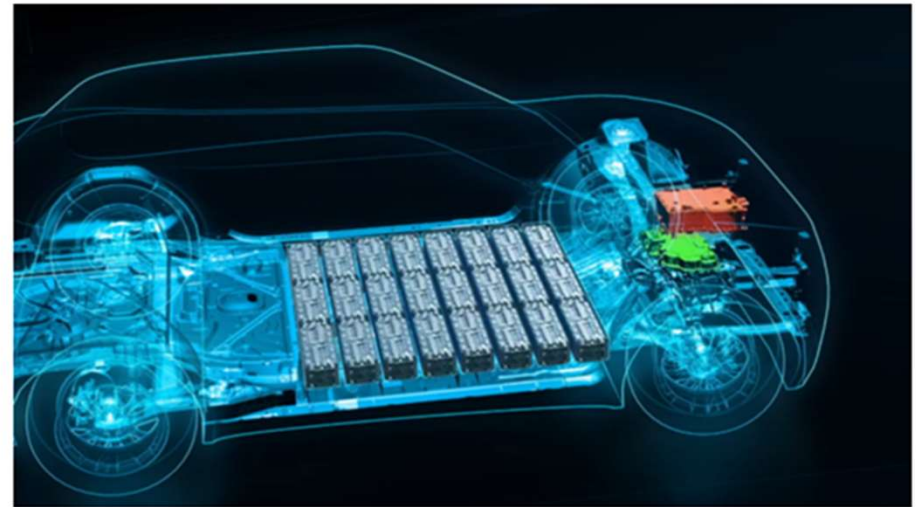

Credit to Stellantis

GENERAL STRUCTURE OF MMC


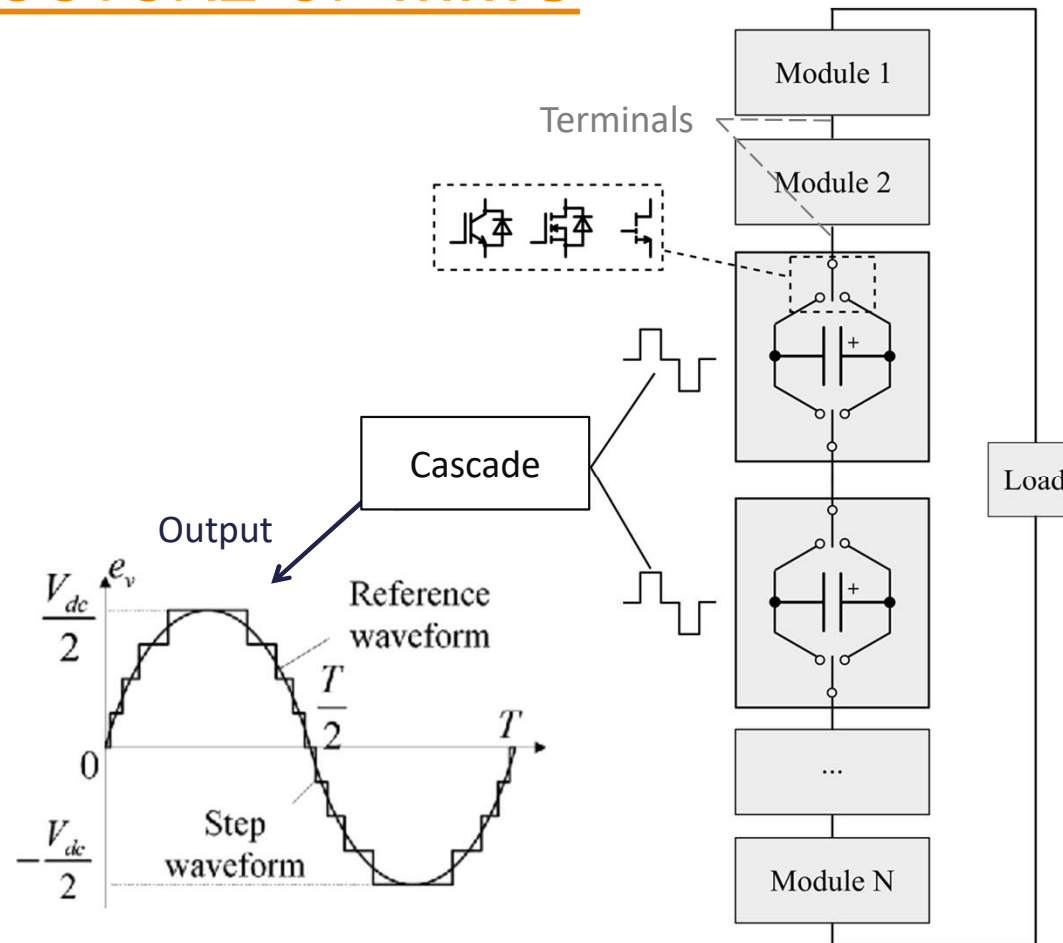



TABLE OF CONTENT

- Introduction
 - General structure of modular multilevel converter (MMC)
 - Evolution to enable parallel connectivity
- Working principle of Direction-Selective Parallel Structure
 - Structure
 - Conduction mechanism
 - Paralleling mechanism
- Results
- Conclusion

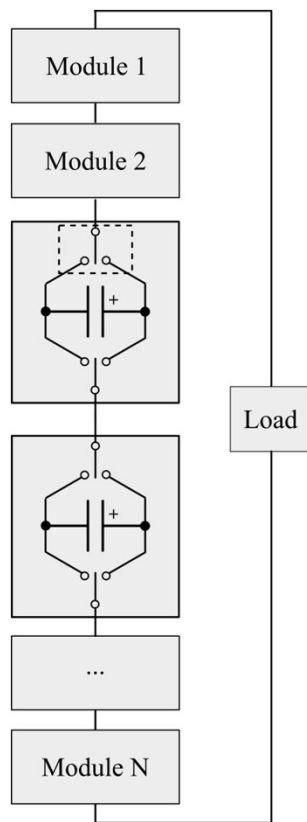
EVOLUTION: ENABLING PARALLEL CONNECTIVITY



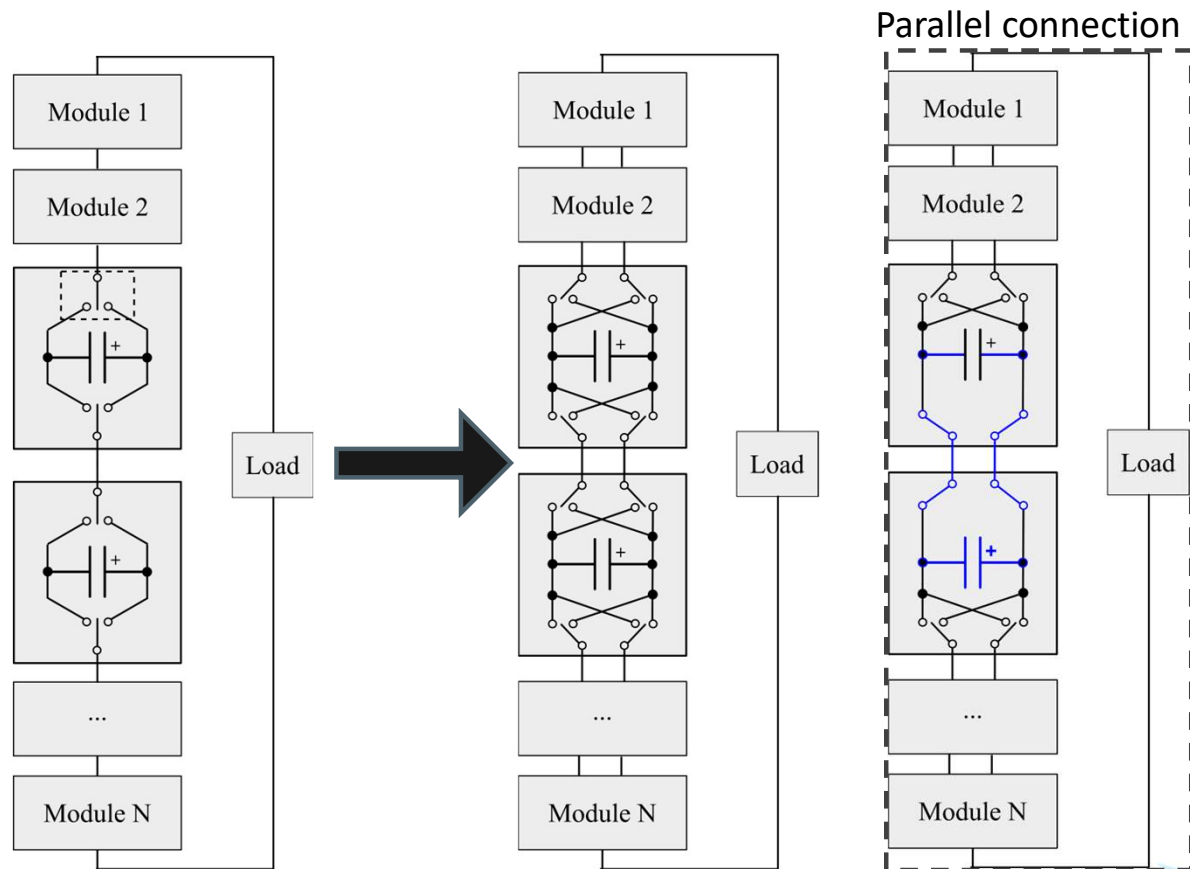EVOLUTION: ENABLING PARALLEL CONNECTIVITY



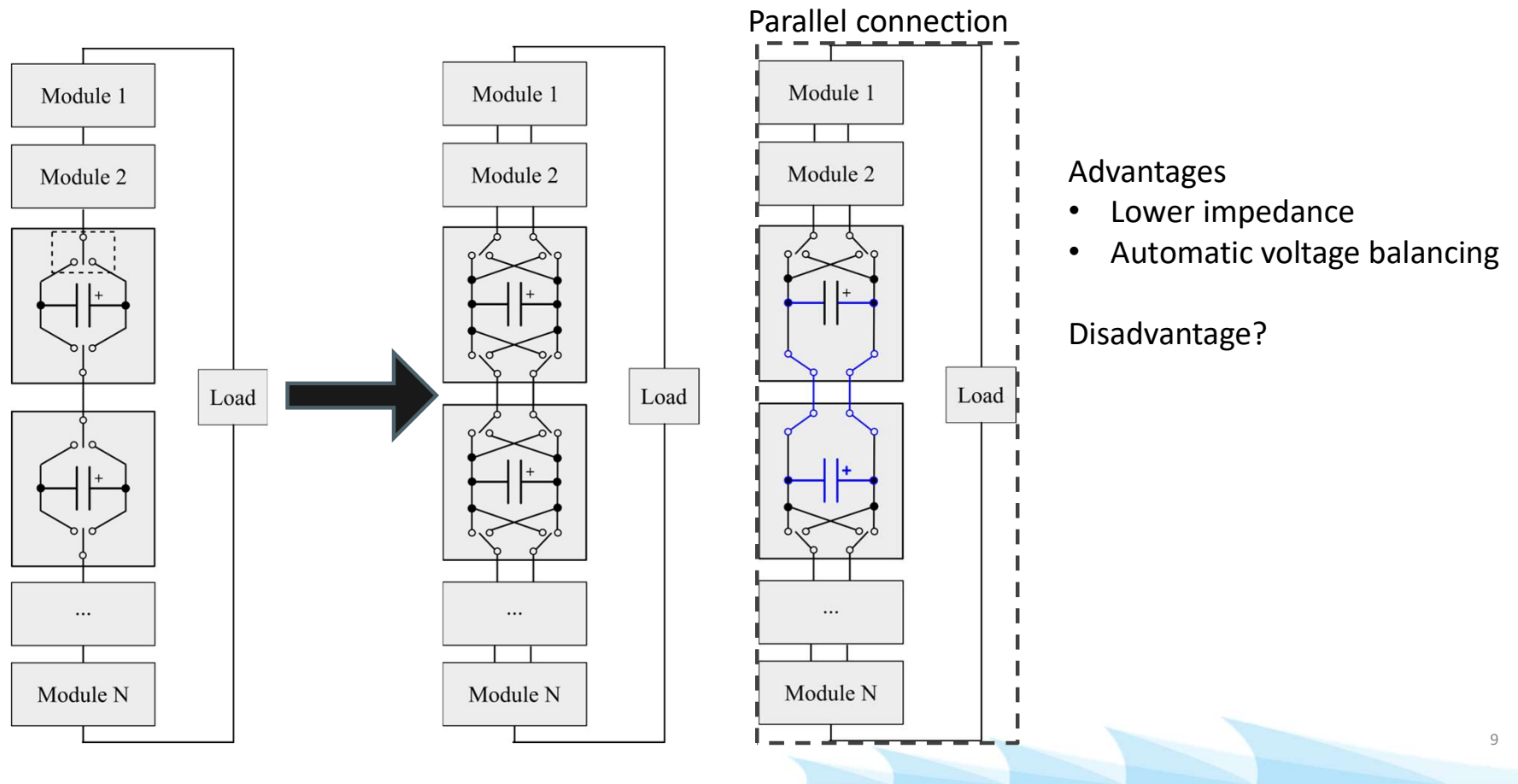
EVOLUTION: ENABLING PARALLEL CONNECTIVITY



STORY TIME




CASCADED DOUBLE H BRIDGE CIRCUIT

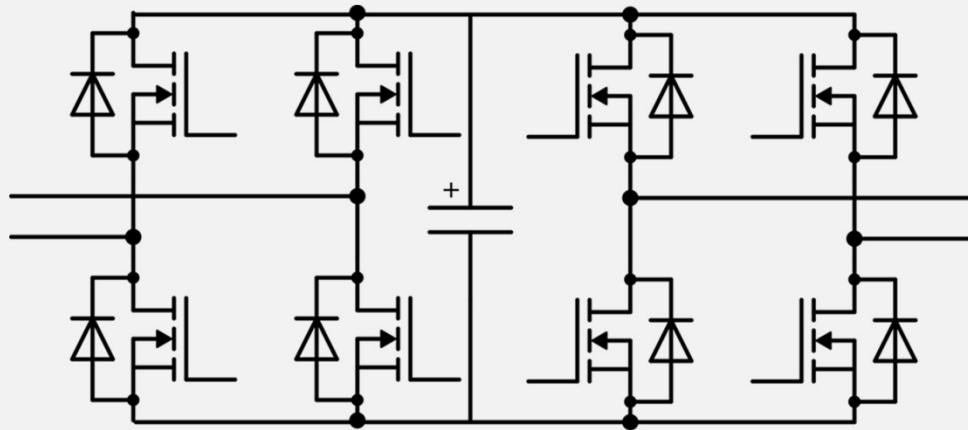


Cascaded double H bridge circuit

Disadvantages: \$\$\$\$

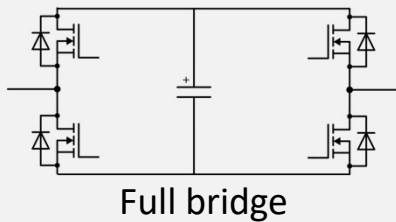

VS

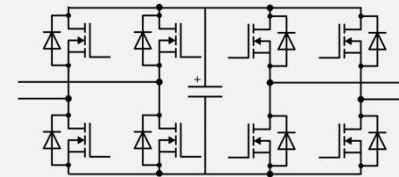


Cascaded double H bridge (CH2B)

Topology	Transistor count	Parallel mode?	Output polarity
Full-bridge	4	No	Bipolar
CH2B	8	Yes	Bipolar

TABLE OF CONTENT


- Introduction
 - General structure of modular multilevel converter (MMC)
 - Evolution to enable parallel connectivity
- Working principle of Direction-Selective Parallel Structure
 - Structure
 - Conduction mechanism
 - Paralleling mechanism
- Results
- Conclusion

CASCADED DOUBLE H BRIDGE CIRCUIT

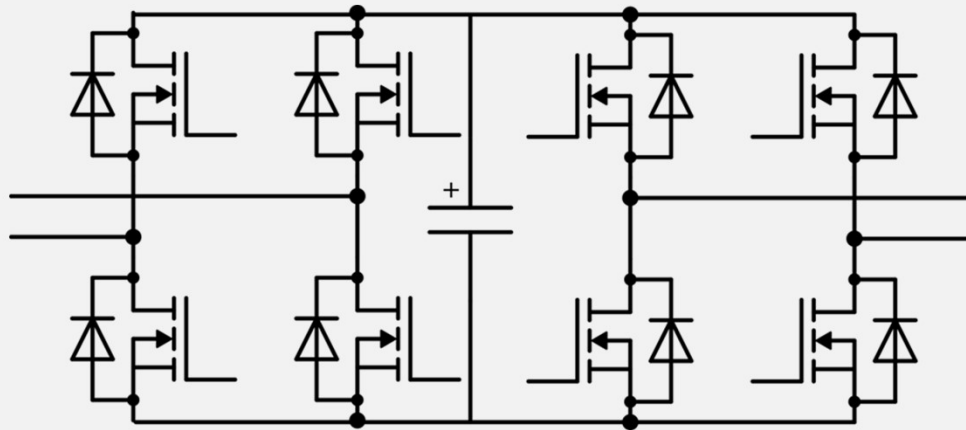


Cascaded double H bridge circuit

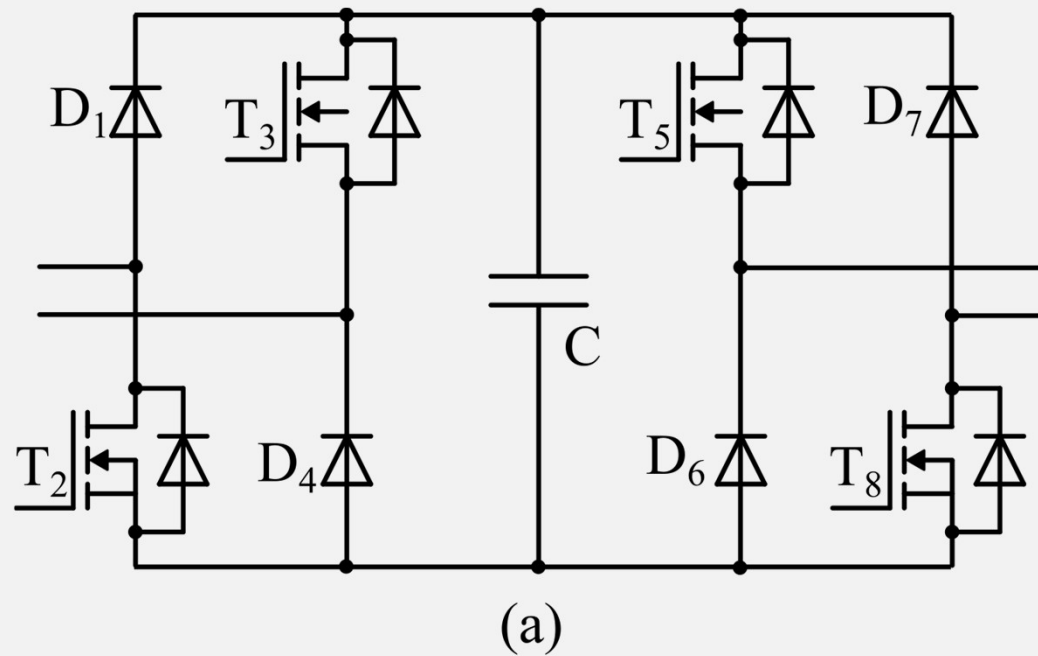DIRECTION-SELECTIVE PARALLEL MODULE STRUCTURE



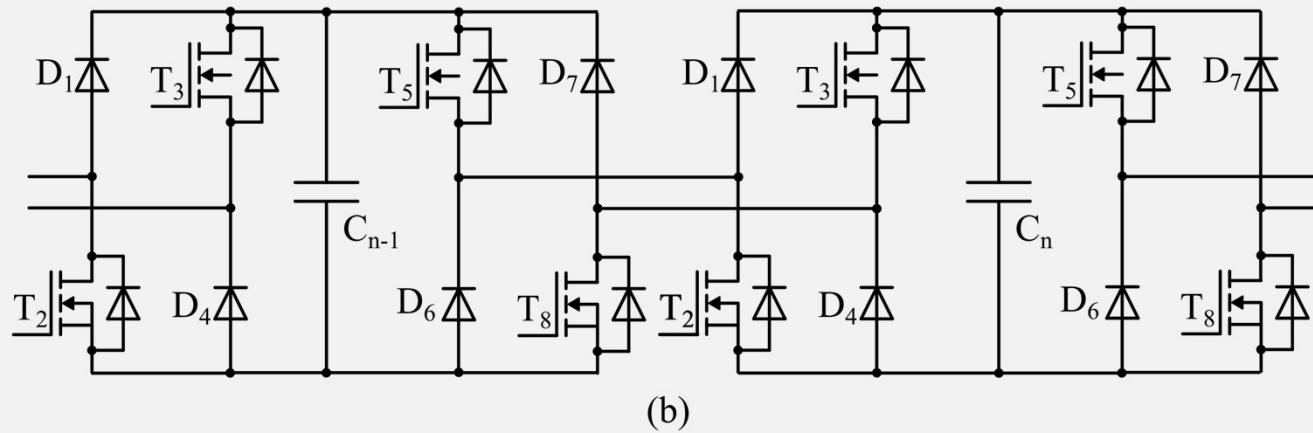
(a) Topology. (b) Connection. (c) Series connection. (d) Parallel connection. (e) Bypass connection

DIRECTION-SELECTIVE PARALLEL MODULE STRUCTURE




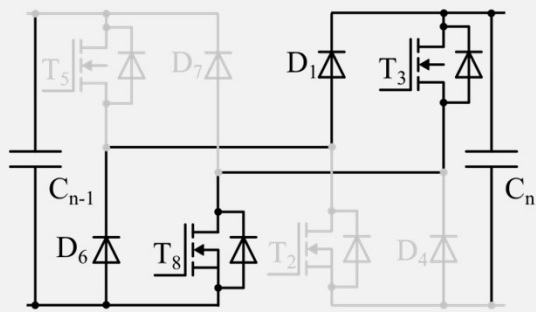(a) Topology. (b) Connection. (c) Series connection. (d) Parallel connection. (e) Bypass connection


DIRECTION-SELECTIVE PARALLEL MODULE STRUCTURE




(c1)

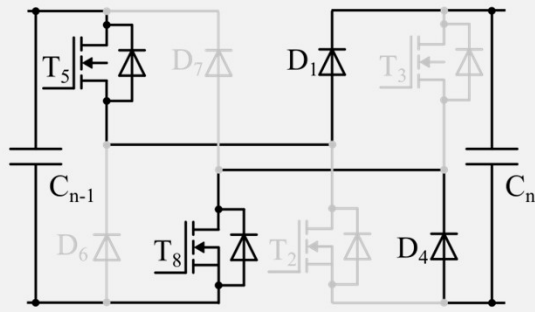


(d1)

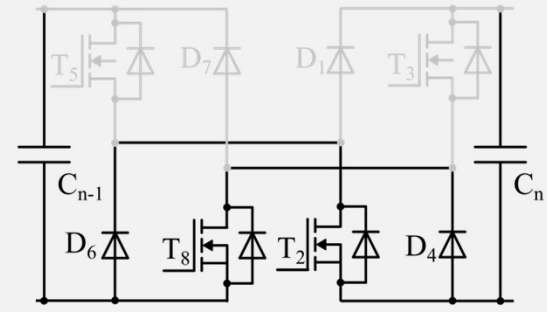


(e1)

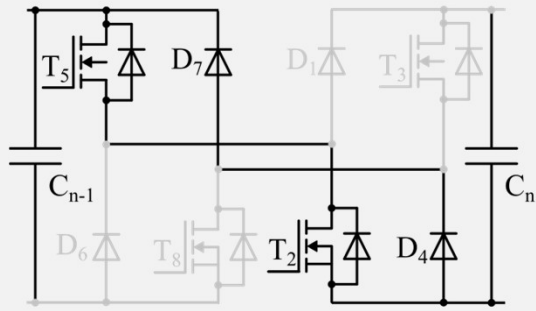

(c2)

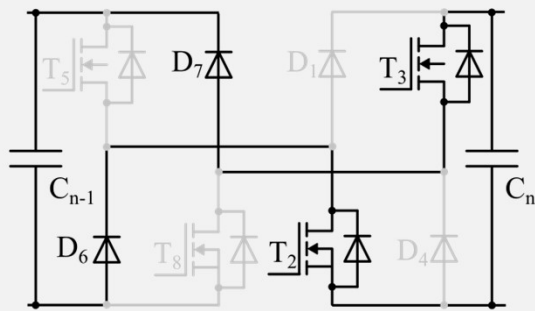

(d2)

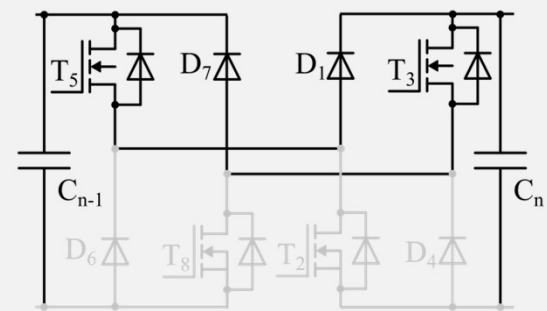

(e2)





(a) Topology. (b) Connection. (c) Series connection. (d) Parallel connection. (e) Bypass connection

TABLE OF CONTENT

- Introduction
 - General structure of modular multilevel converter (MMC)
 - Evolution to enable parallel connectivity
- Working principle of Direction-Selective Parallel Structure
 - Structure
 - Conduction mechanism
 - Paralleling mechanism
- Results
- Conclusion





DIRECTION-SELECTIVE PARALLEL MODULE STRUCTURE:

CURRENT PATH

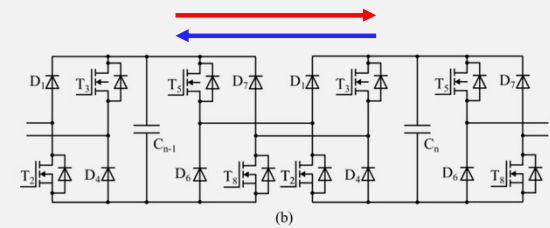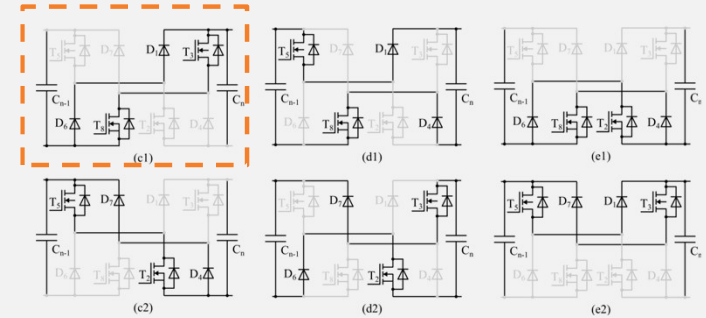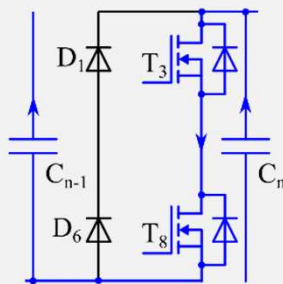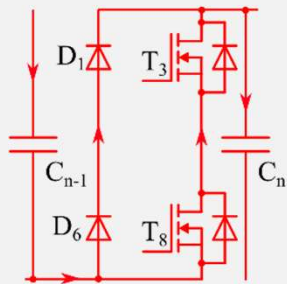




DIRECTION-SELECTIVE PARALLEL MODULE STRUCTURE:

CURRENT PATH

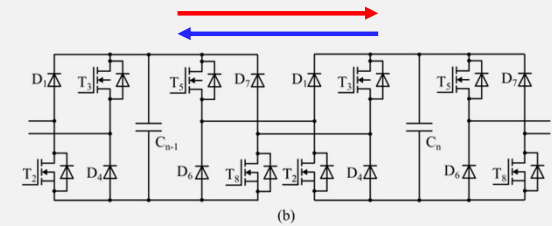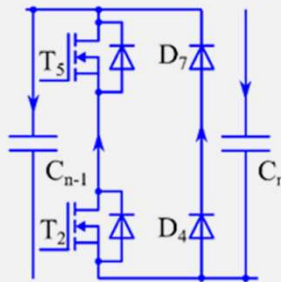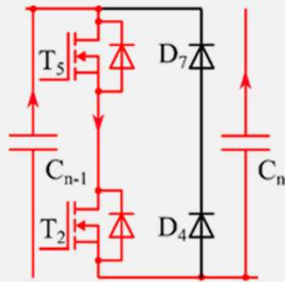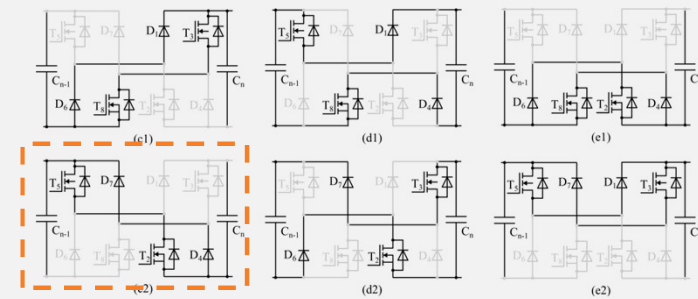




DIRECTION-SELECTIVE PARALLEL MODULE STRUCTURE:

CURRENT PATH

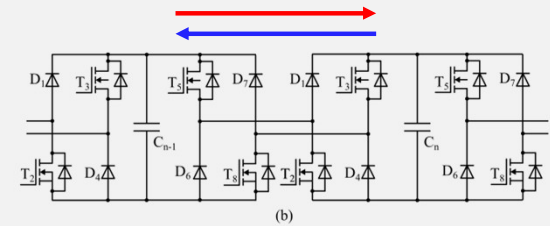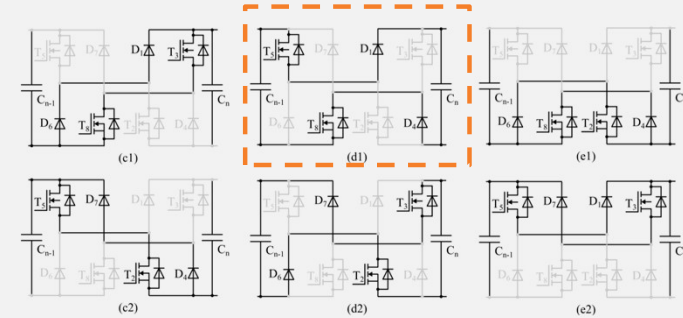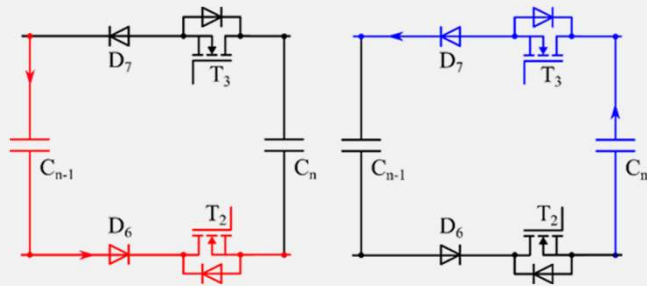




DIRECTION-SELECTIVE PARALLEL MODULE STRUCTURE:

CURRENT PATH

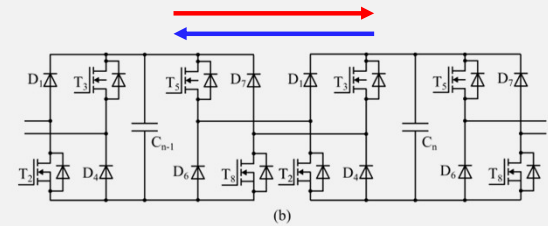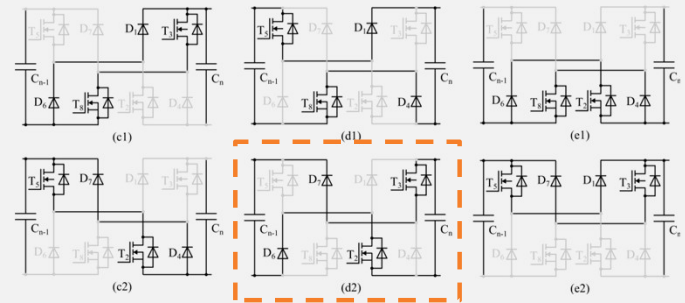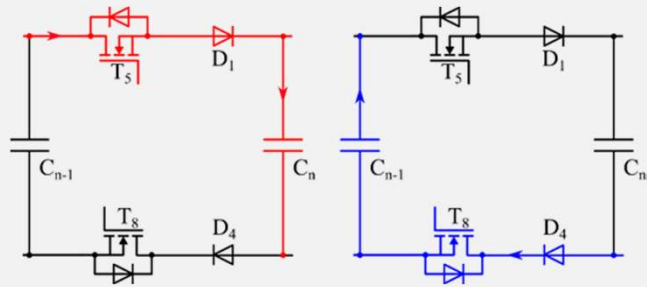

DIRECTION-SELECTIVE PARALLEL MODULE STRUCTURE:

CURRENT PATH

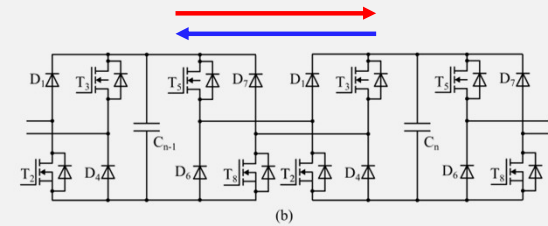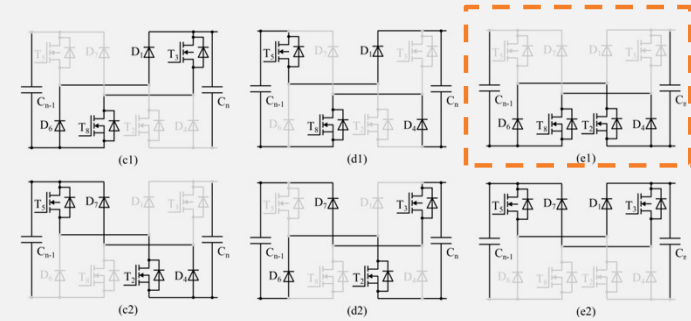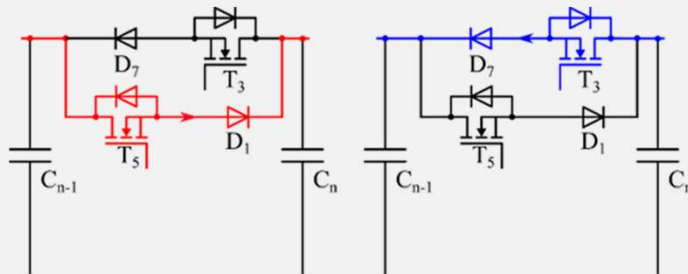

DIRECTION-SELECTIVE PARALLEL MODULE STRUCTURE:

CURRENT PATH


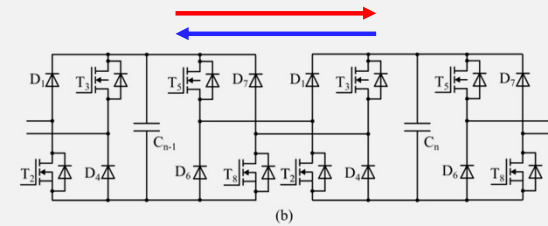
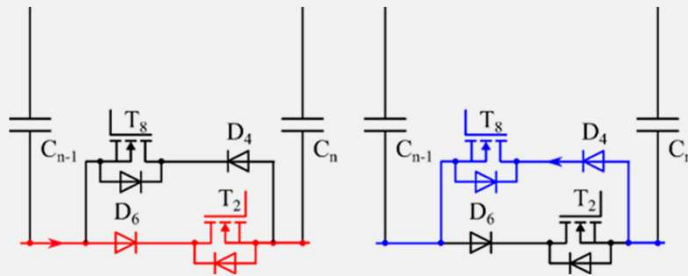
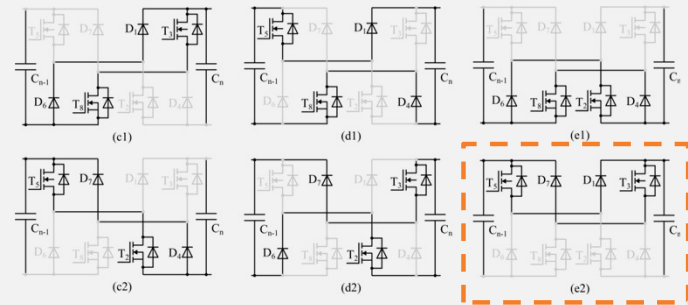
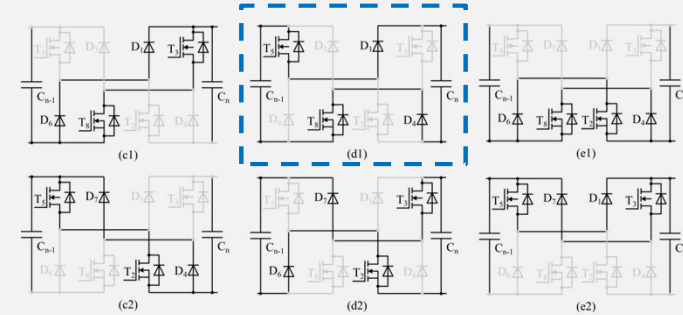


TABLE OF CONTENT

- Introduction
 - General structure of modular multilevel converter (MMC)
 - Evolution to enable parallel connectivity
- Working principle of Direction-Selective Parallel Structure
 - Structure
 - Conduction mechanism
 - Paralleling mechanism
- Results
- Conclusion

DIRECTION-SELECTIVE PARALLEL MODULE STRUCTURE:

PARALLELING LOOP

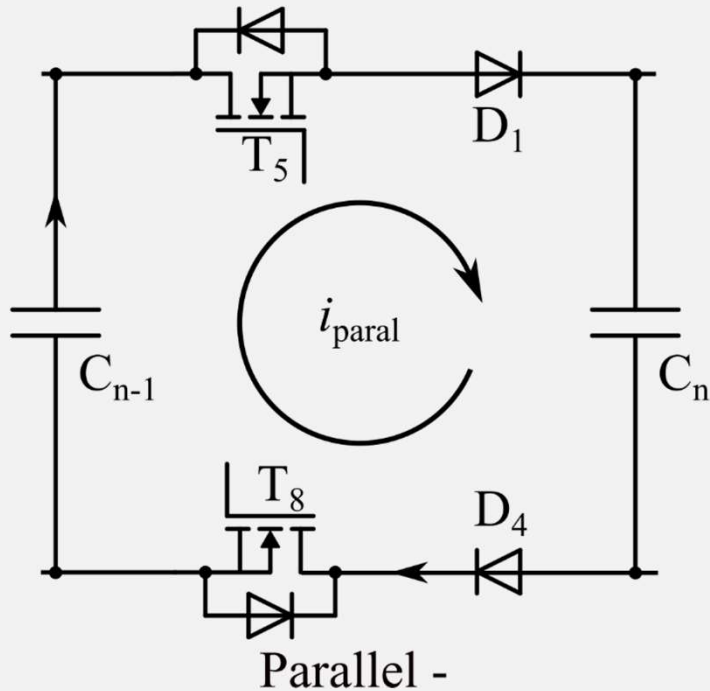

DIRECTION-SELECTIVE PARALLEL MODULE STRUCTURE:

PARALLELING LOOP

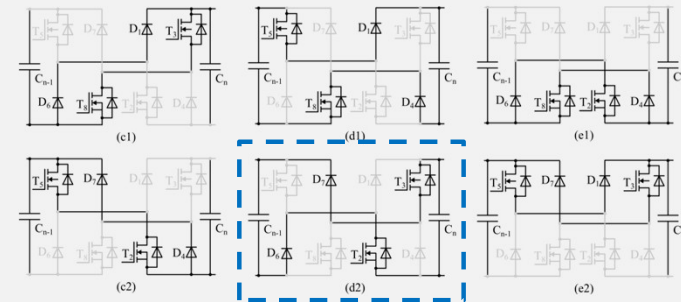
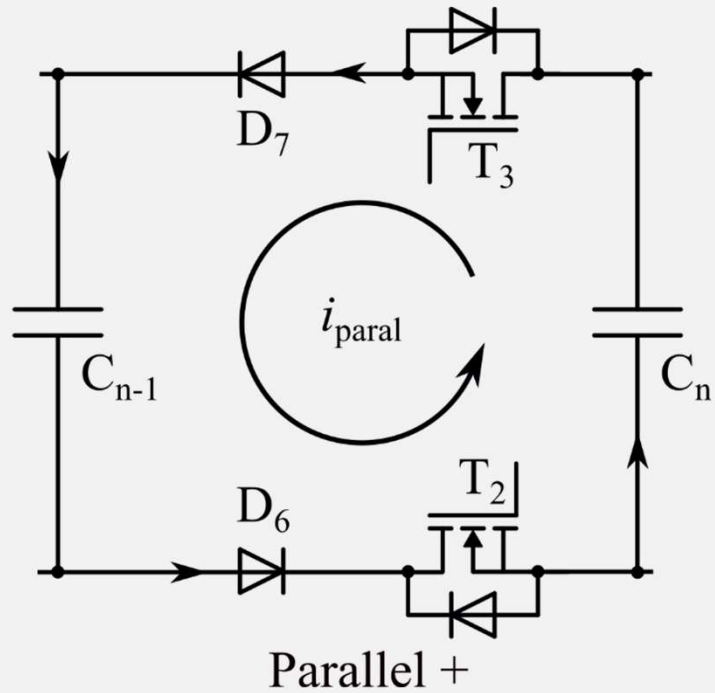


TABLE OF CONTENT

- Introduction
 - General structure of modular multilevel converter (MMC)
 - Evolution to enable parallel connectivity
- Working principle of Direction-Selective Parallel Structure
 - Structure
 - Conduction mechanism
 - Paralleling mechanism
- **Results**
- Conclusion

SIMULATION RESULTS

Trial info

- Module number: 3
- Power supply: 100 V to module #2 with 10 m Ω impedance
- Module voltage: 100 V
- Load: 10 Ω + 100 mH


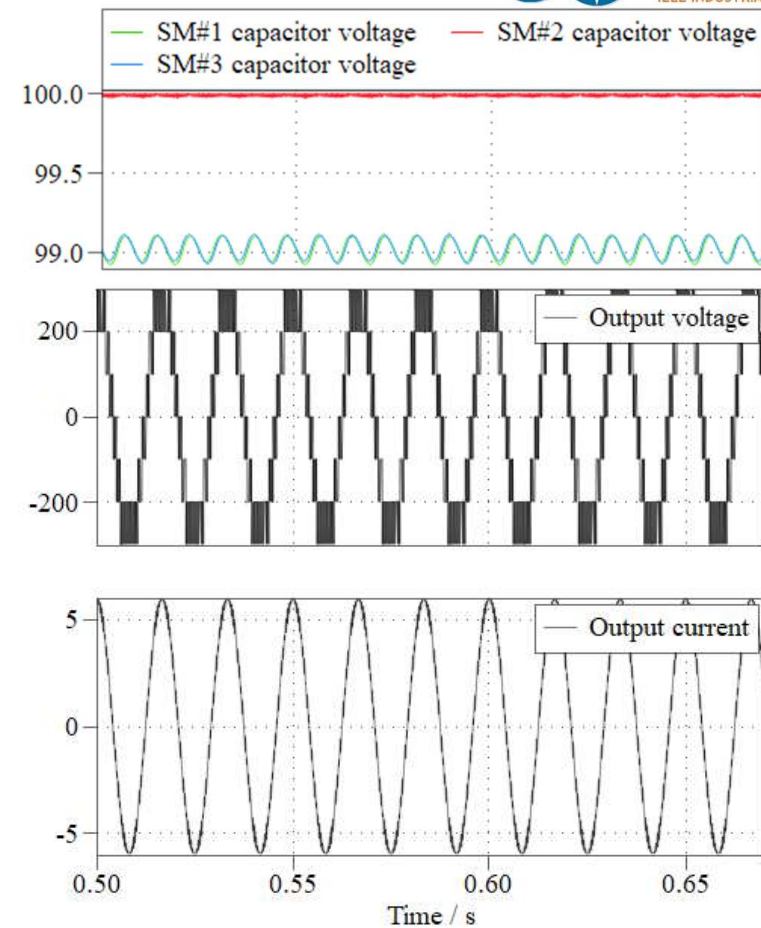


TABLE OF CONTENT


- Introduction
 - General structure of modular multilevel converter (MMC)
 - Evolution to enable parallel connectivity
- Working principle of Direction-Selective Parallel Structure
 - Structure
 - Conduction mechanism
 - Paralleling mechanism
- Results
- Conclusion

CONCLUSION

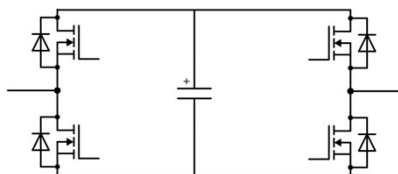


Full bridge

VS

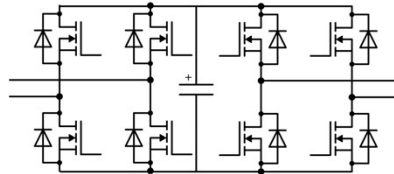

CH2B

VS

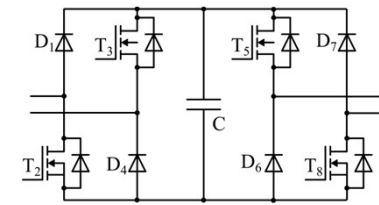

Direction-selective parallel topology

Topology	Transistor	Parallel mode?	Output
Full-bridge	4	No	Bipolar
CH2B	8	Yes	Bipolar
Direction-Selective-Parallel	4	Yes	Bipolar

Thank you!